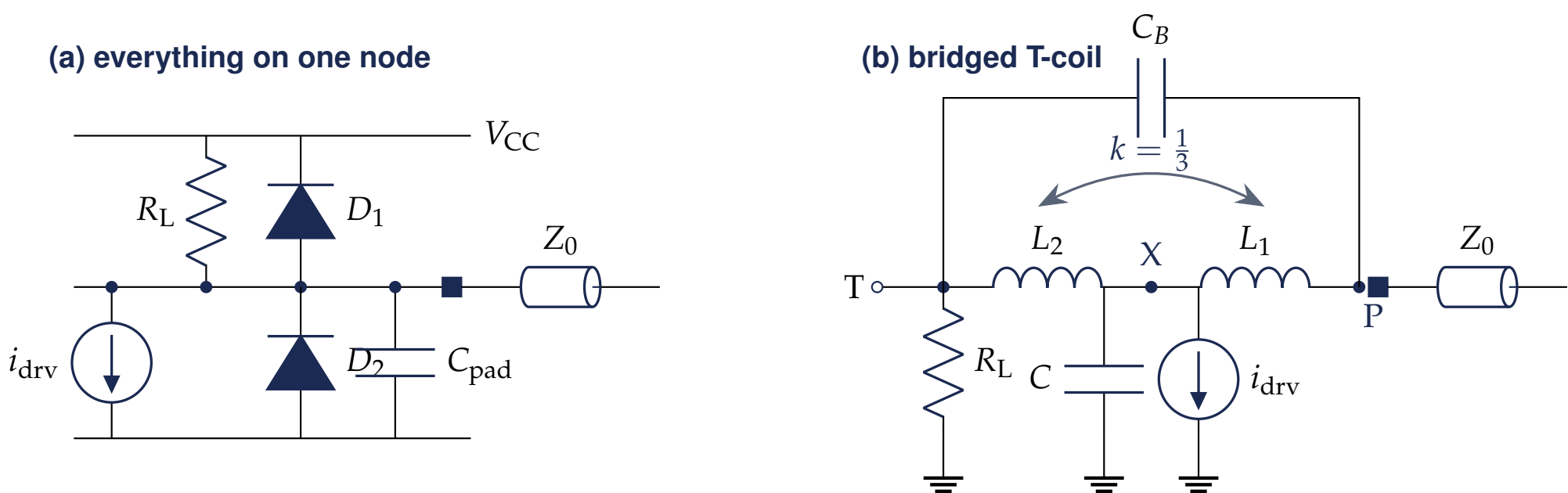
(a) everything on one node
V_{CC}
R_L
D_1
Z_0
i_{drv}
D_2
C_{pad}
(b) bridged T-coil
C_B
$k = \frac{1}{3}$
L_2
X
L_1
Z_0
T
P
R_L
C
i_{drv}